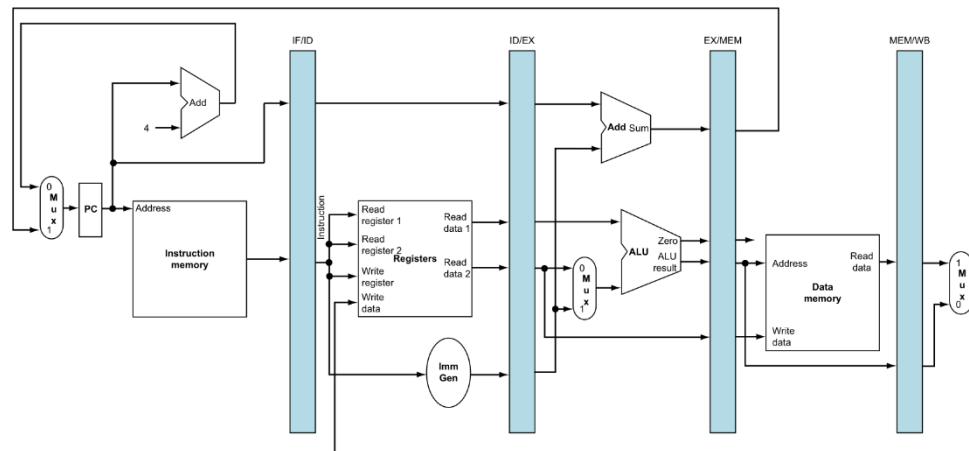



# Processor Architecture

## Pipelined RISC-V Implementation (Part I)



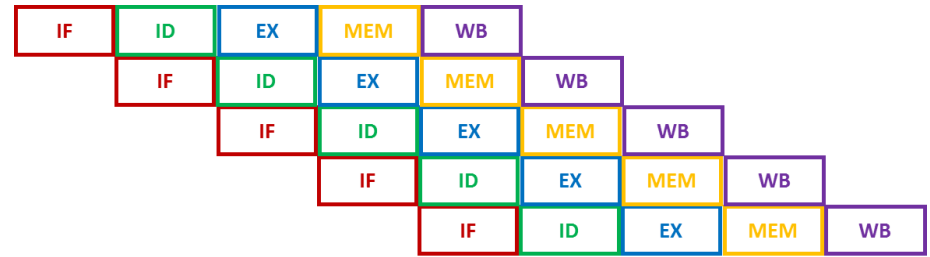
# Module Outline

- **From a Single-Cycle to a Pipelined Implementation**
- **A Pipelined Datapath**
- **A Pipelined Control Path**
- **Module Summary**



# From a Single-Cycle to a Pipelined Implementation


# From Single-Cycle to Pipelining

 


# From Single-Cycle Execution

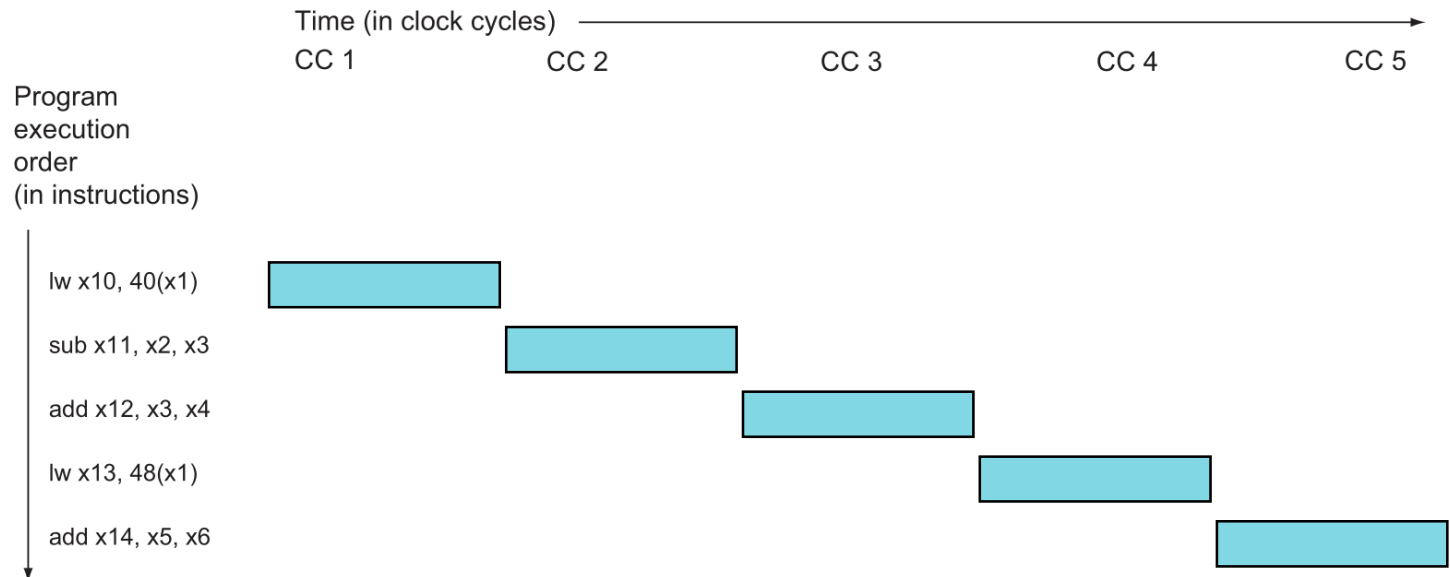
## ■ Instruction sequence

```
lw  x10, 40(x1)
sub x11, x2, x3
add x12, x3, x4
lw  x13, 48(x1)
add x14, x5, x6
```



# Pipelined Execution

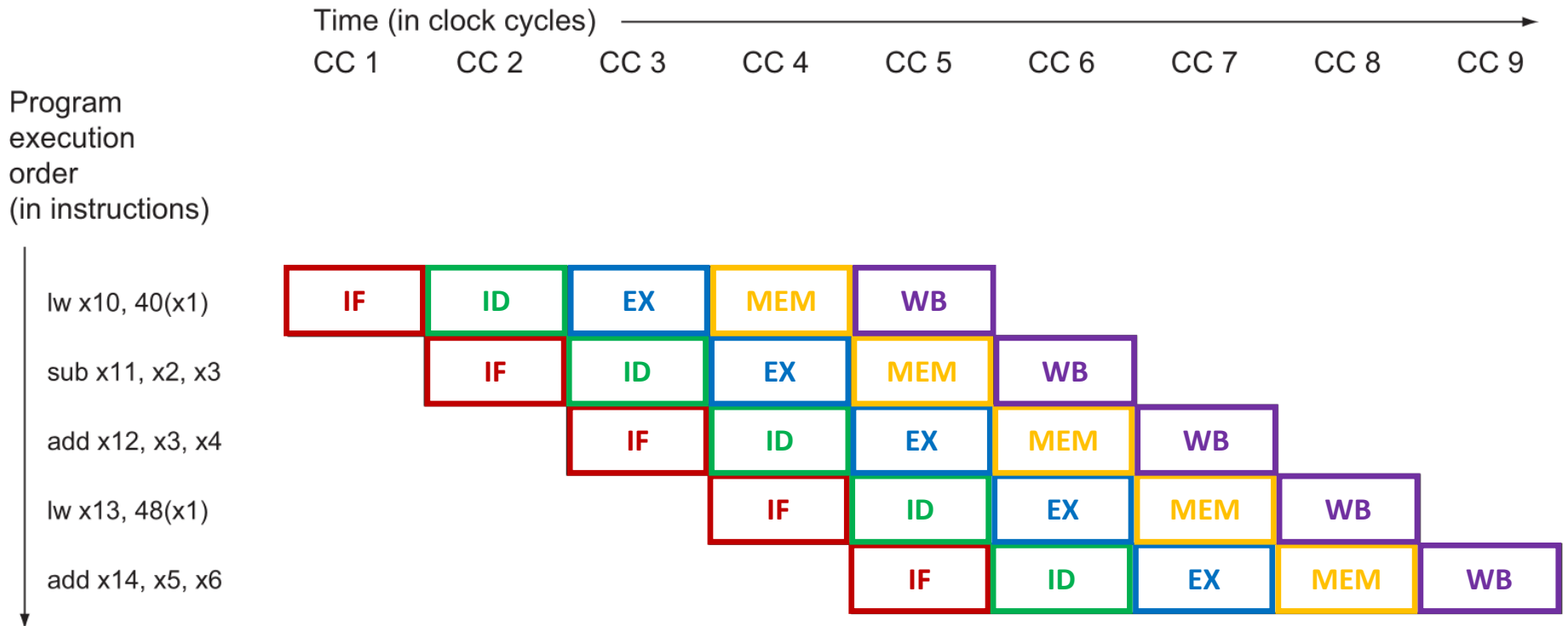

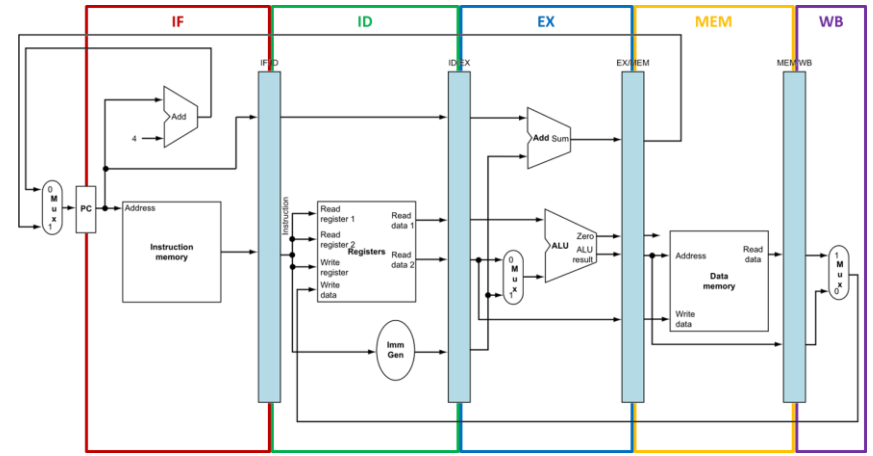

# A Pipelined Datapath

# RISC-V Pipelined Datapath

Instruction fetch


Instruction decode

Execute

Memory

Write back

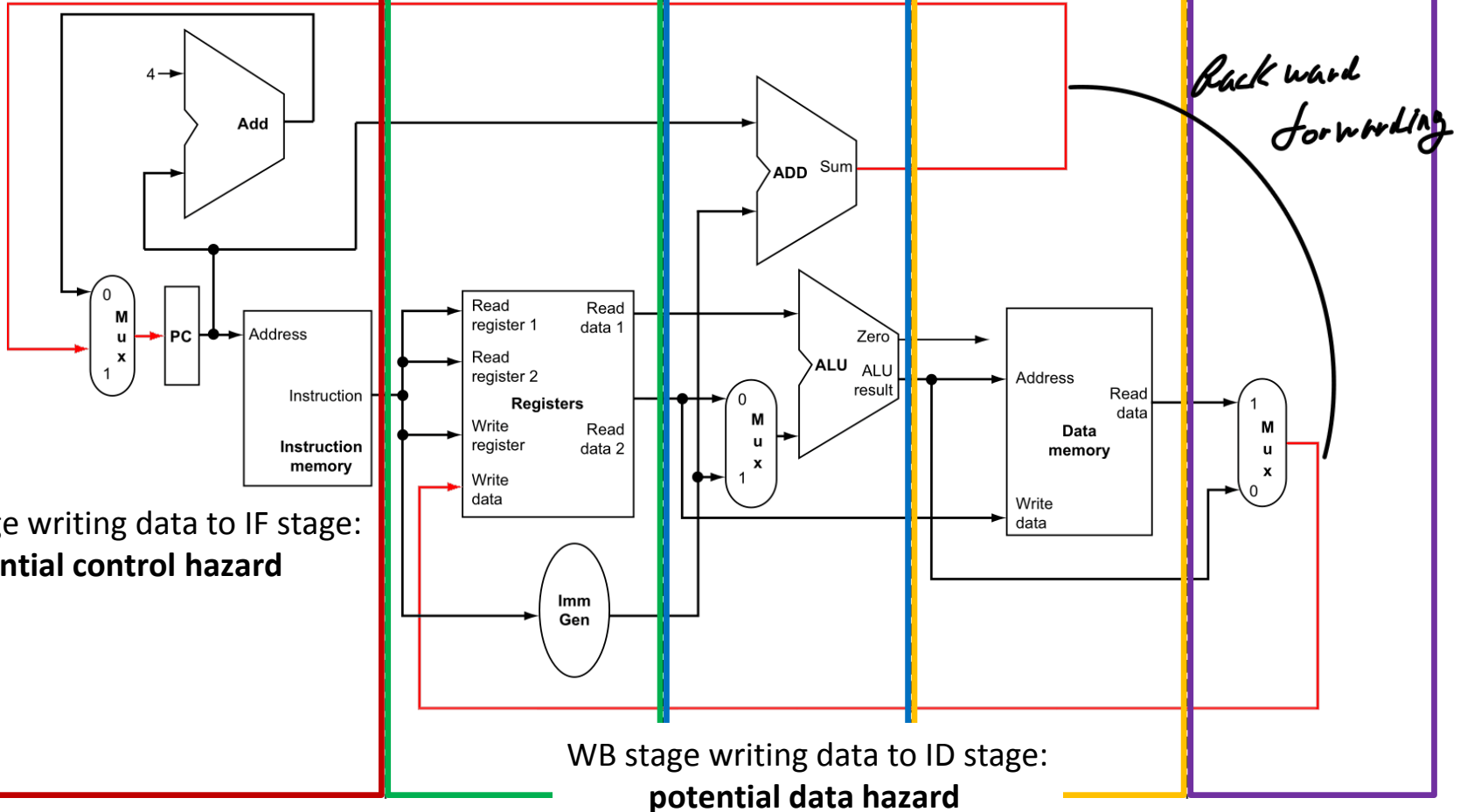
Right-to-left information flow can lead to hazards




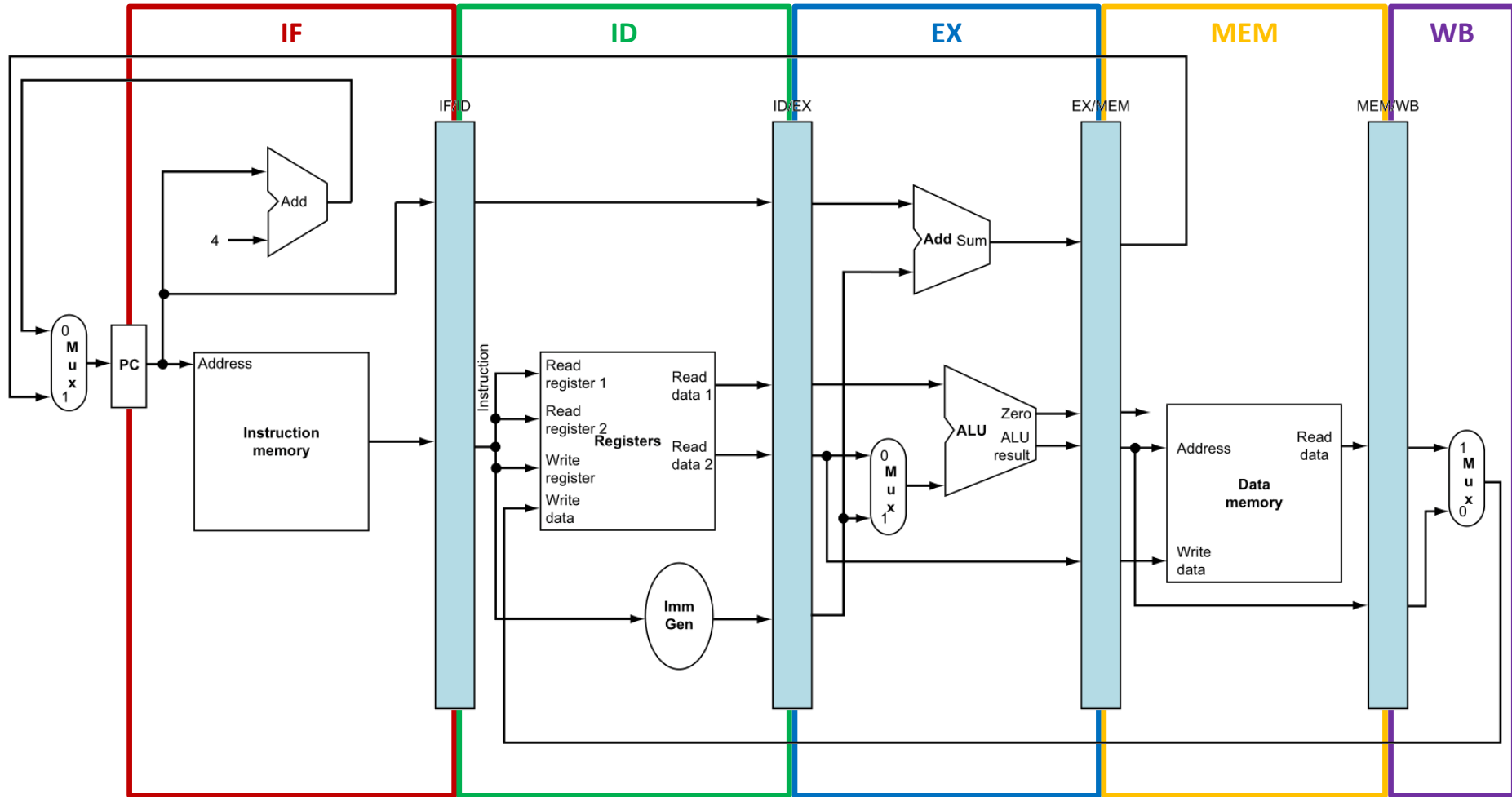
# Pipeline Registers


- Pipeline registers hold information produced in previous cycle




# Pipeline Operation

- Cycle-by-cycle flow of instructions through the pipelined datapath
- “Single-clock-cycle” pipeline diagram
  - Shows pipeline usage in a single cycle
  - Highlight resource used
  - (cf.) “multi-clock-cycle” diagram: graph of operation over time
- Let’s have a look at “single-clock-cycle” diagrams for load & store


# IF for Load

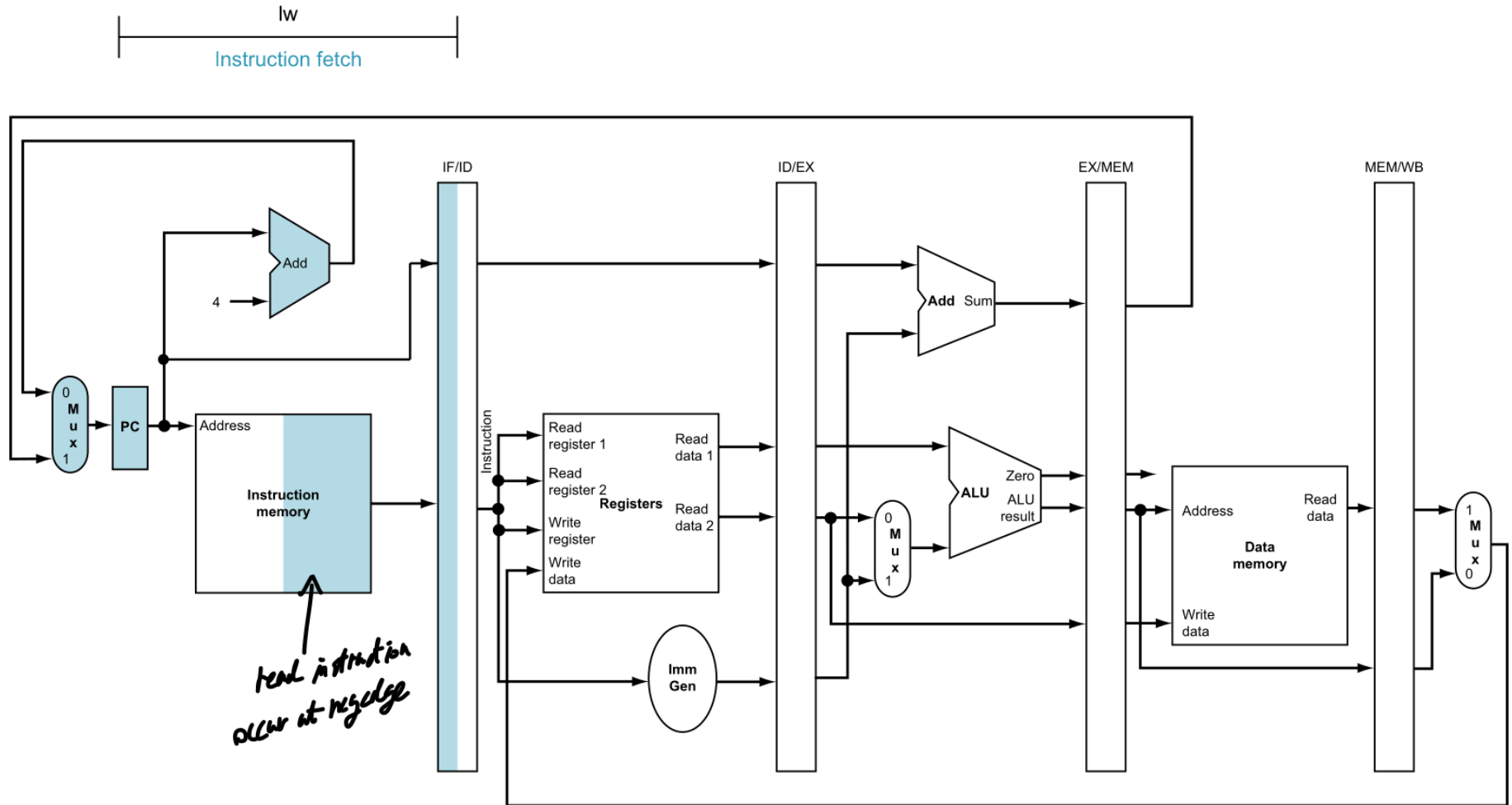


# ID for Load

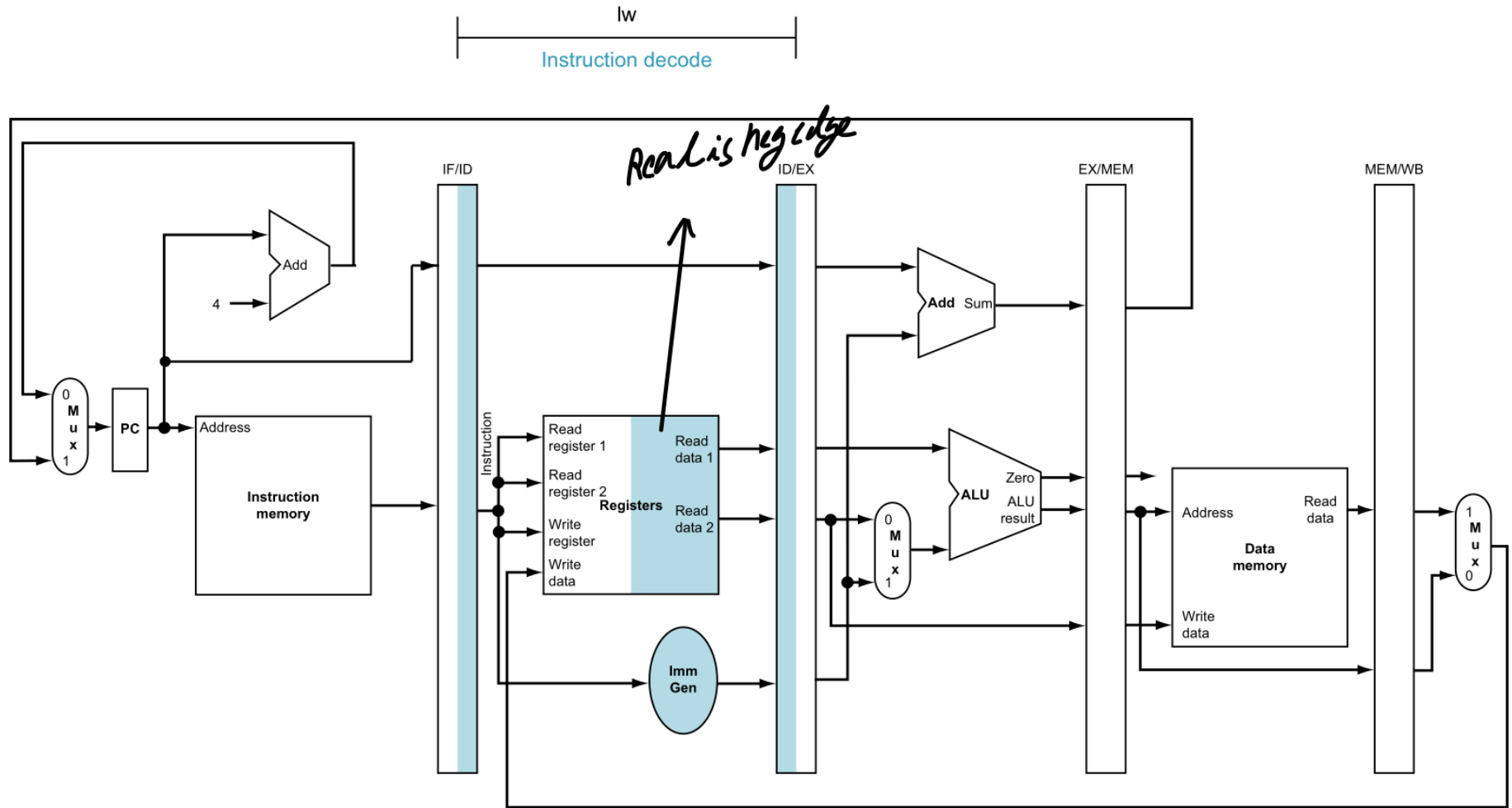


# EX for Load

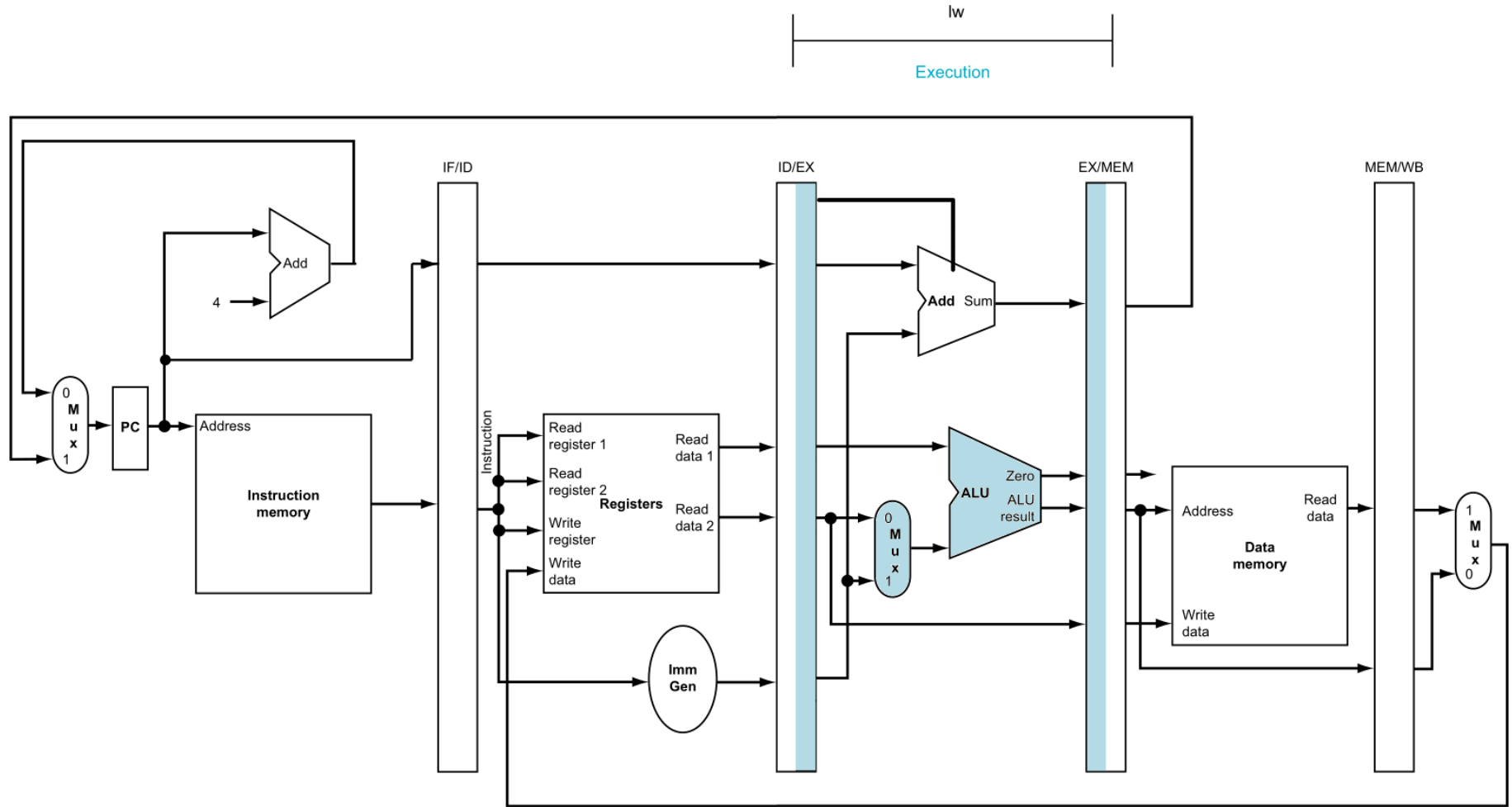


# MEM for Load

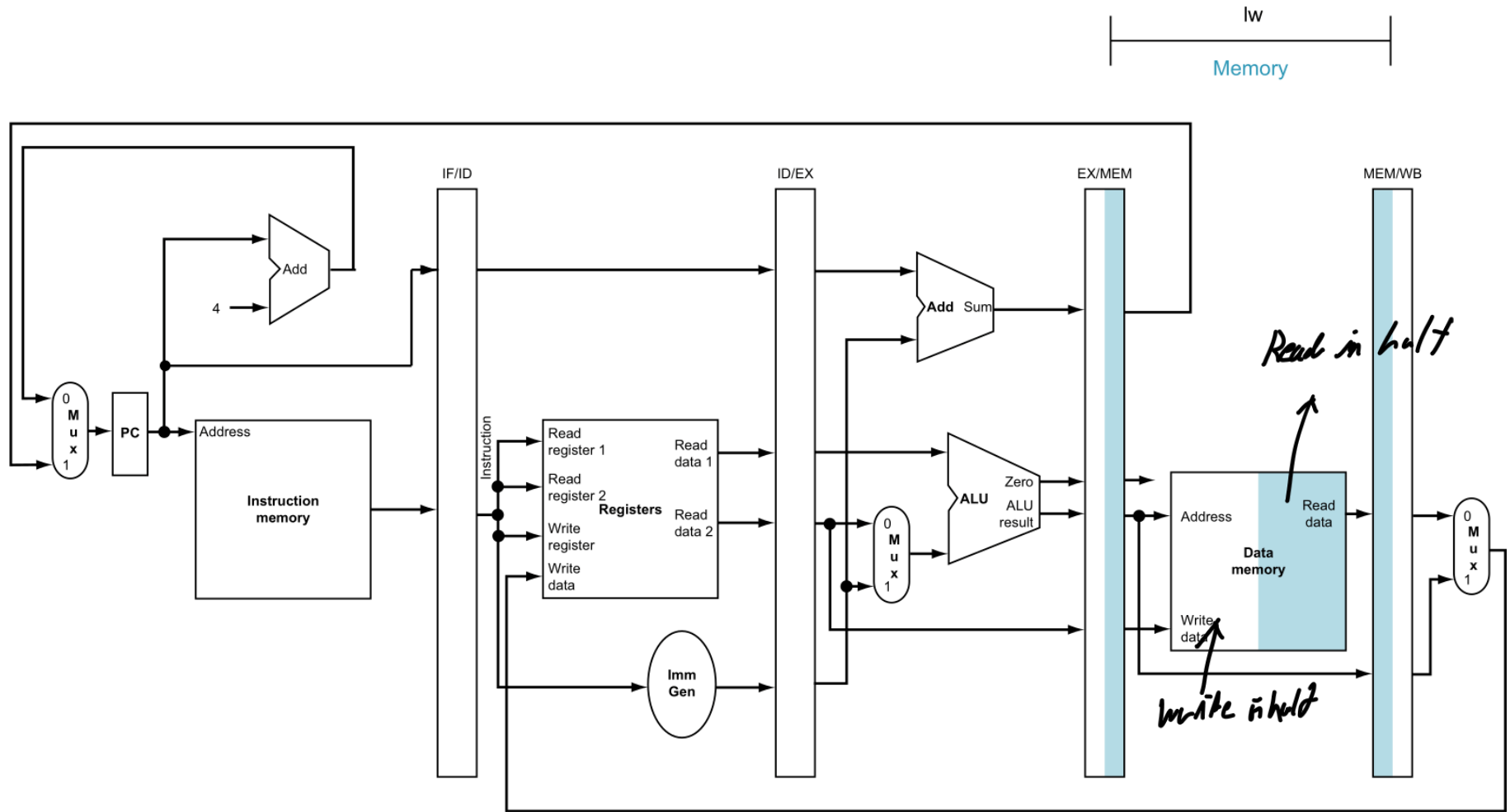

# WB for Load

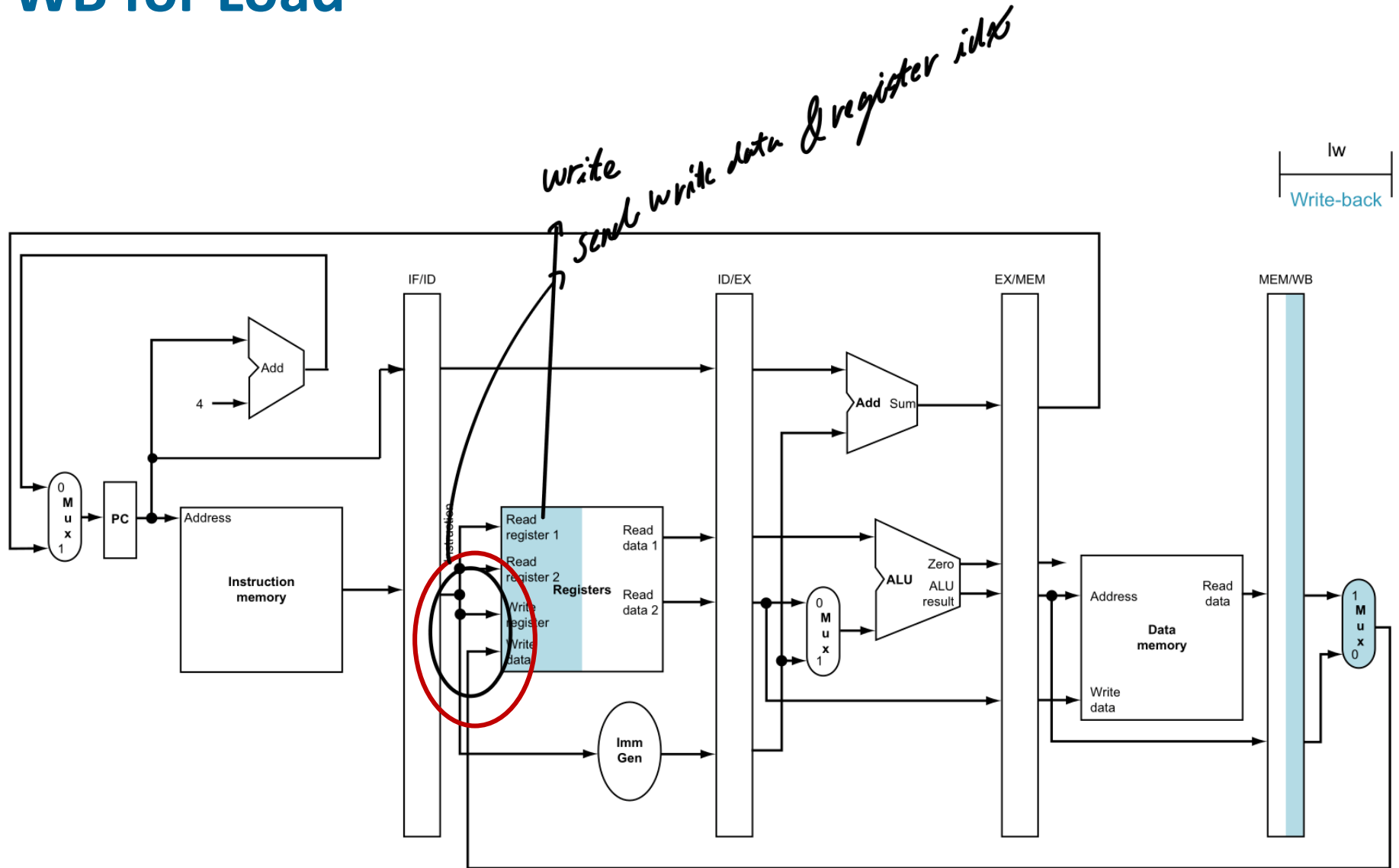



# Corrected Datapath for Load

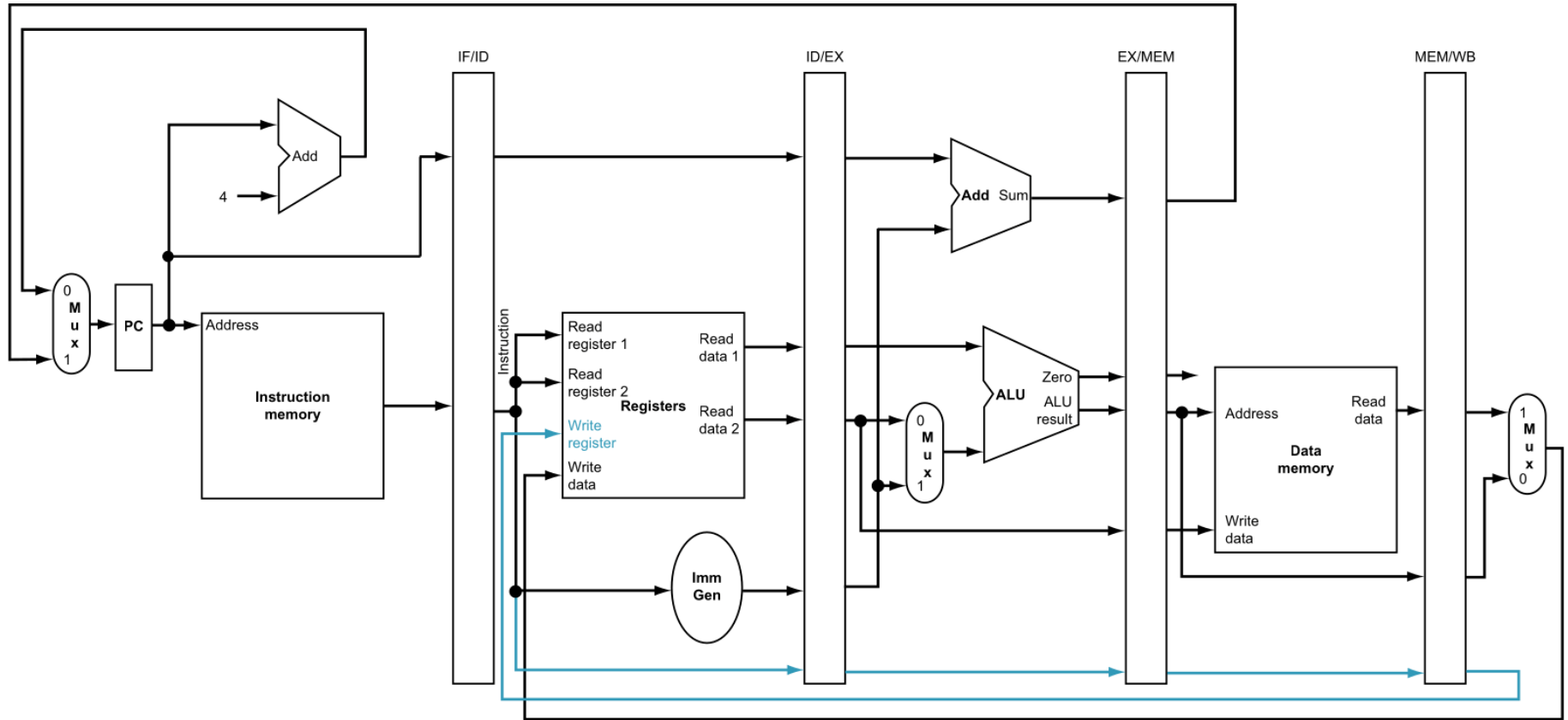



# IF for Store


*read instruction*

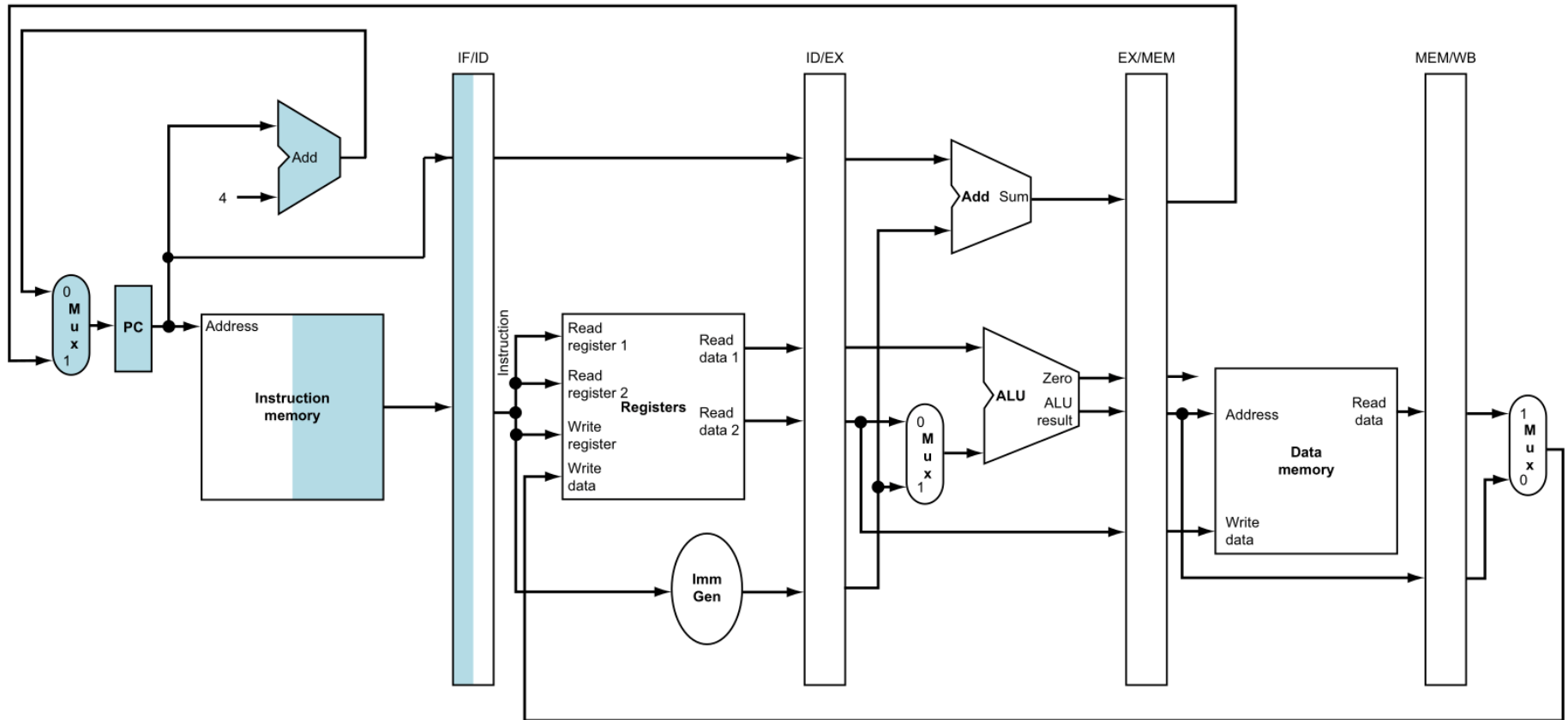 


# ID for Store

*decode & register setting*


SW  
Instruction decode

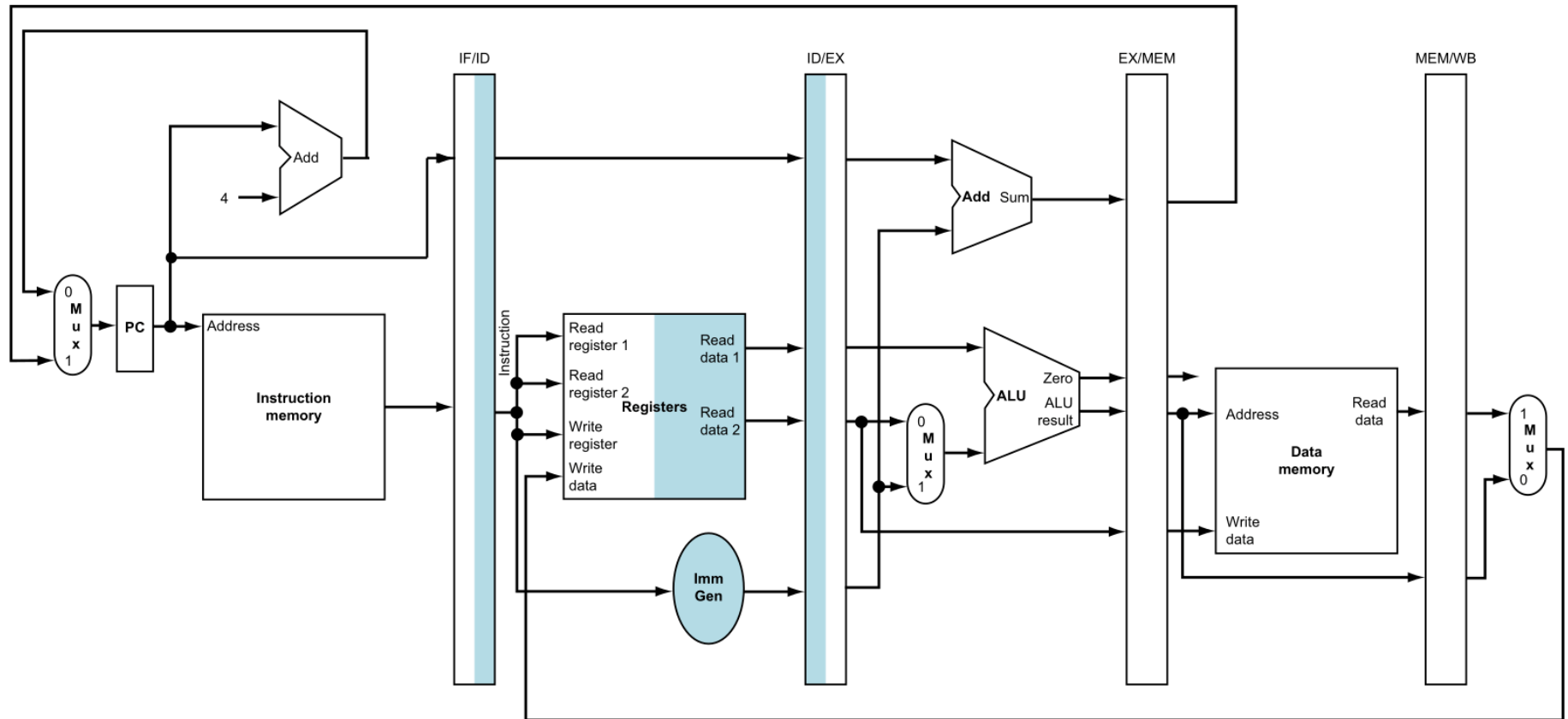


# EX for Store

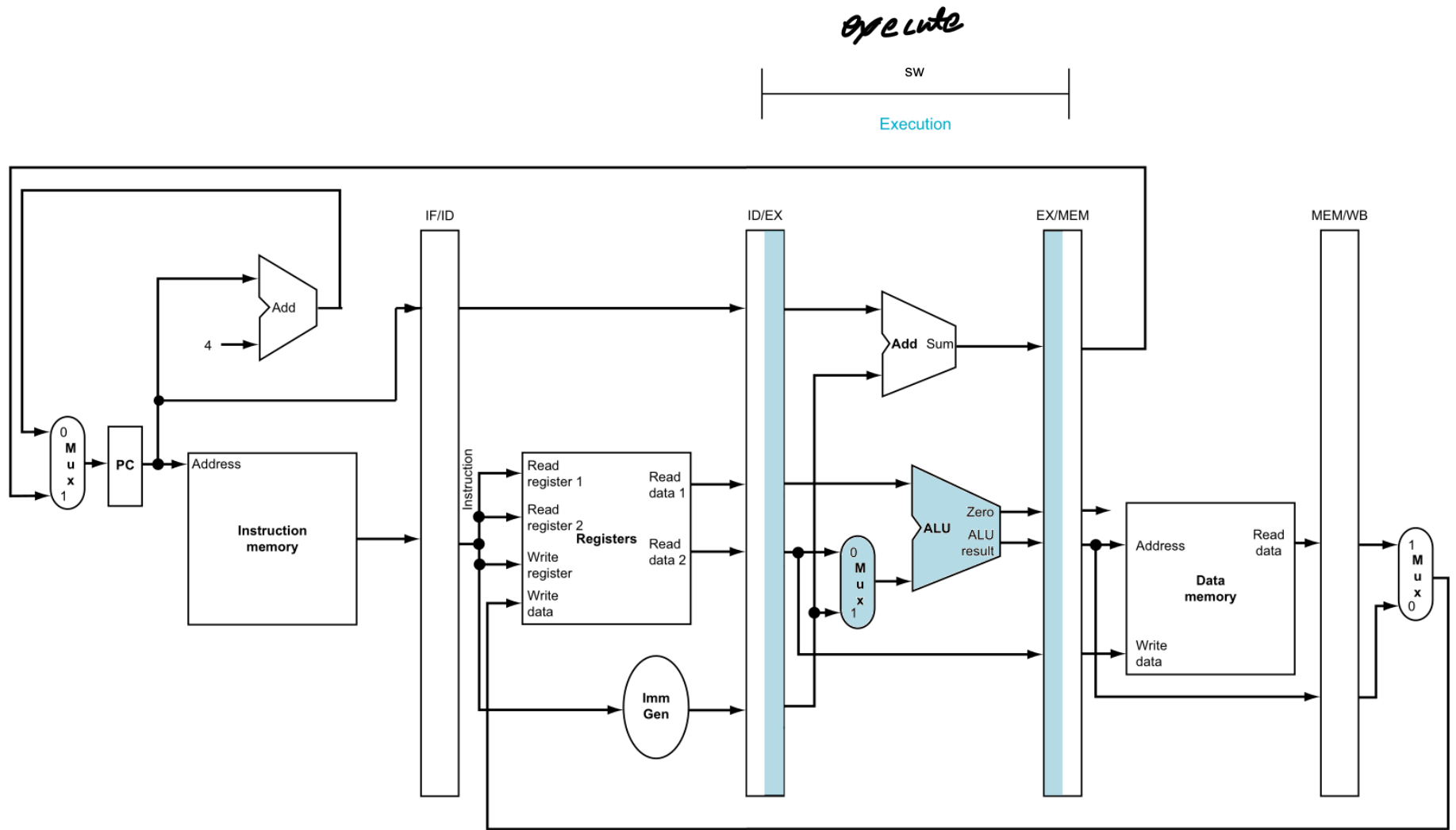


# MEM for Store

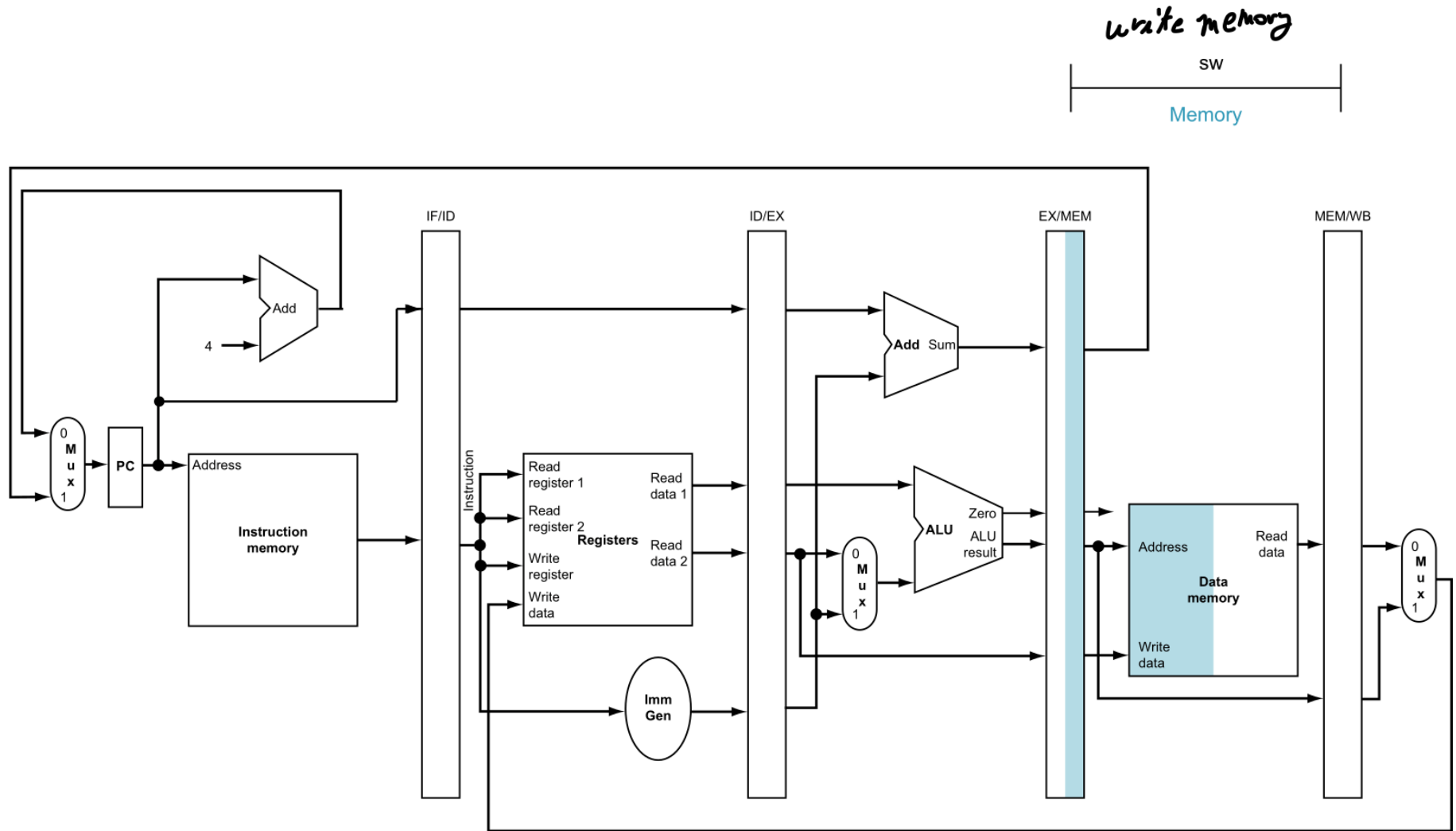


# WB for Store

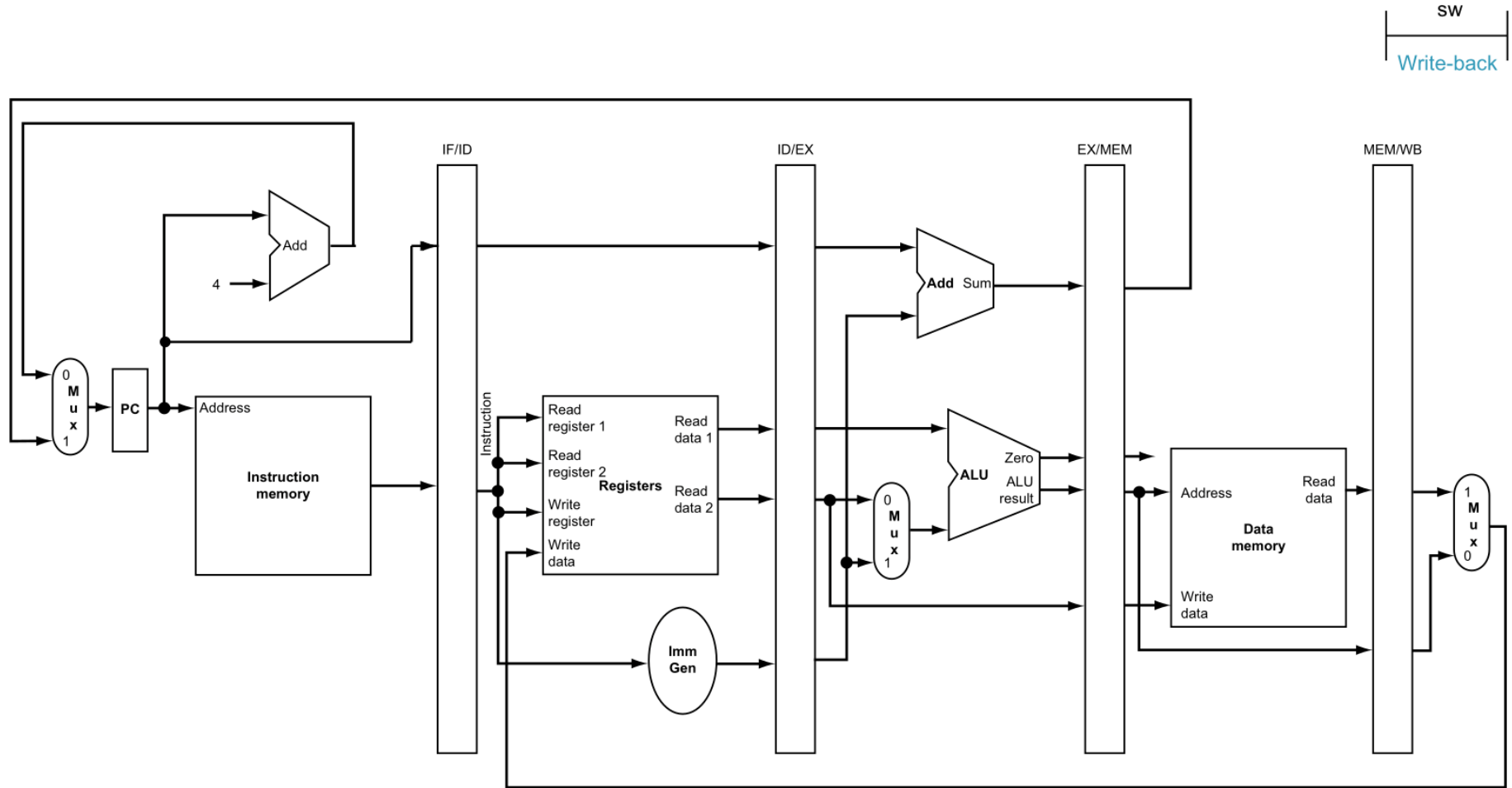

# Pipelined Execution

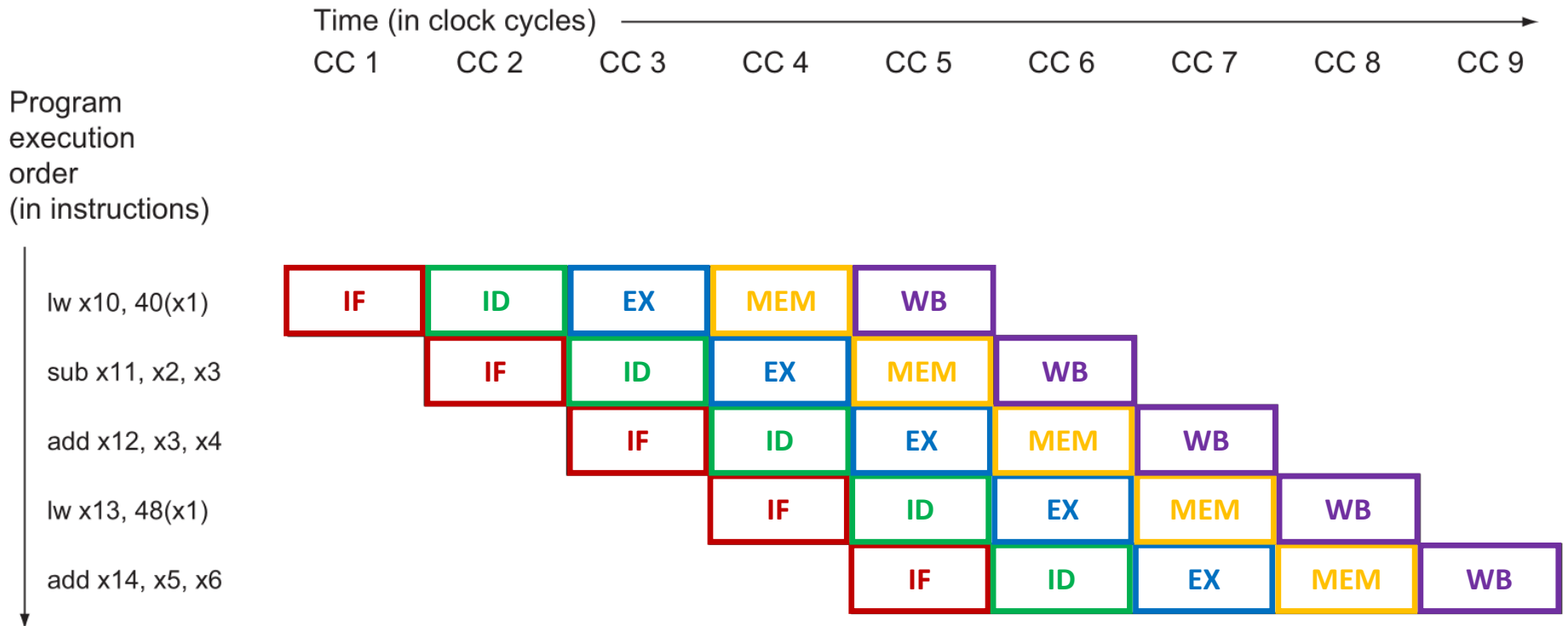

# Pipelined Execution

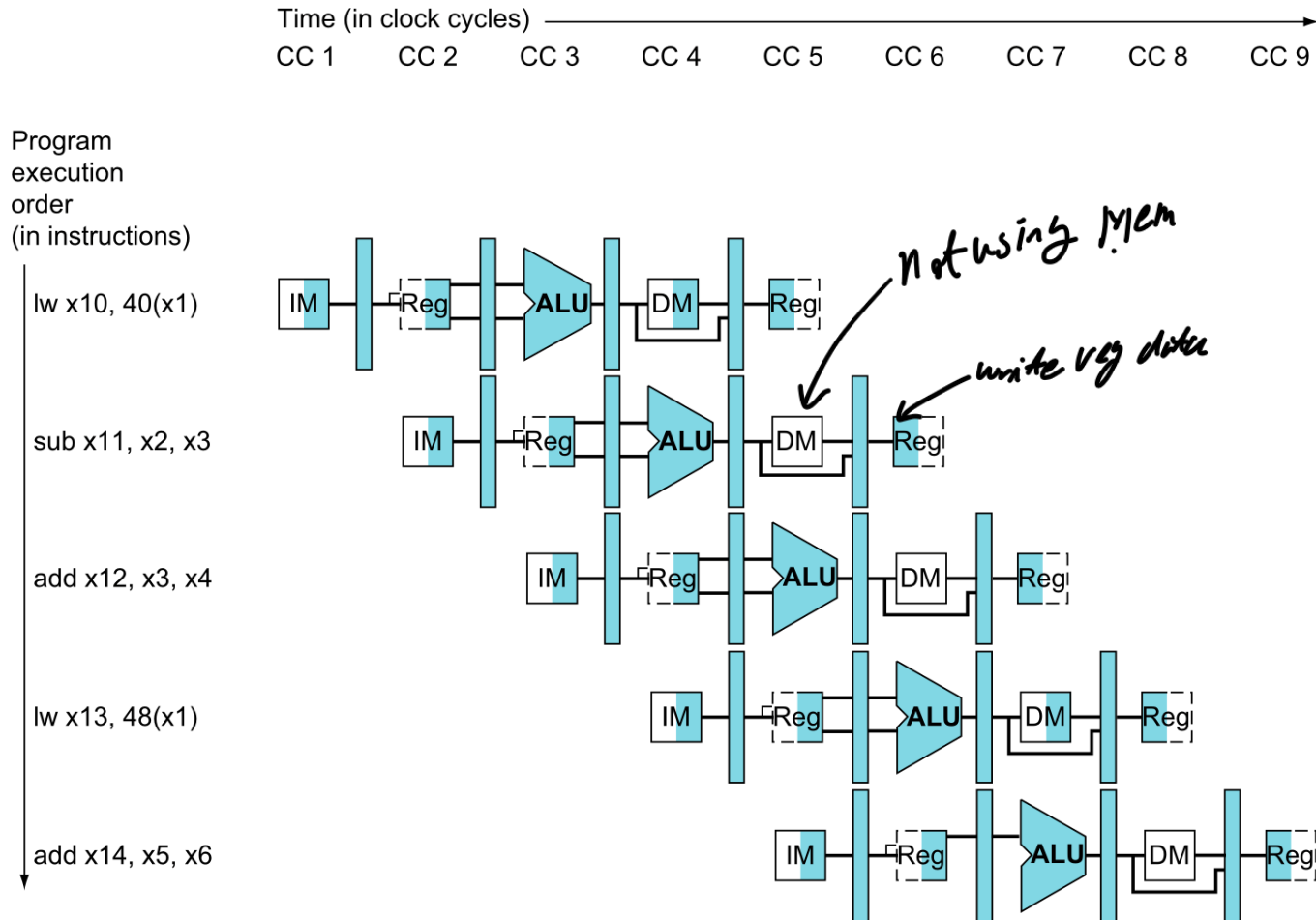



# Single-Cycle Pipeline Diagram

- State of pipeline in a given cycle

*backward half*


CC 5

lw x10, 40(x1)	WB
sub x11, x2, x3	MEM
add x12, x3, x4	EX
lw x13, 48(x1)	ID
add x14, x5, x6	IF

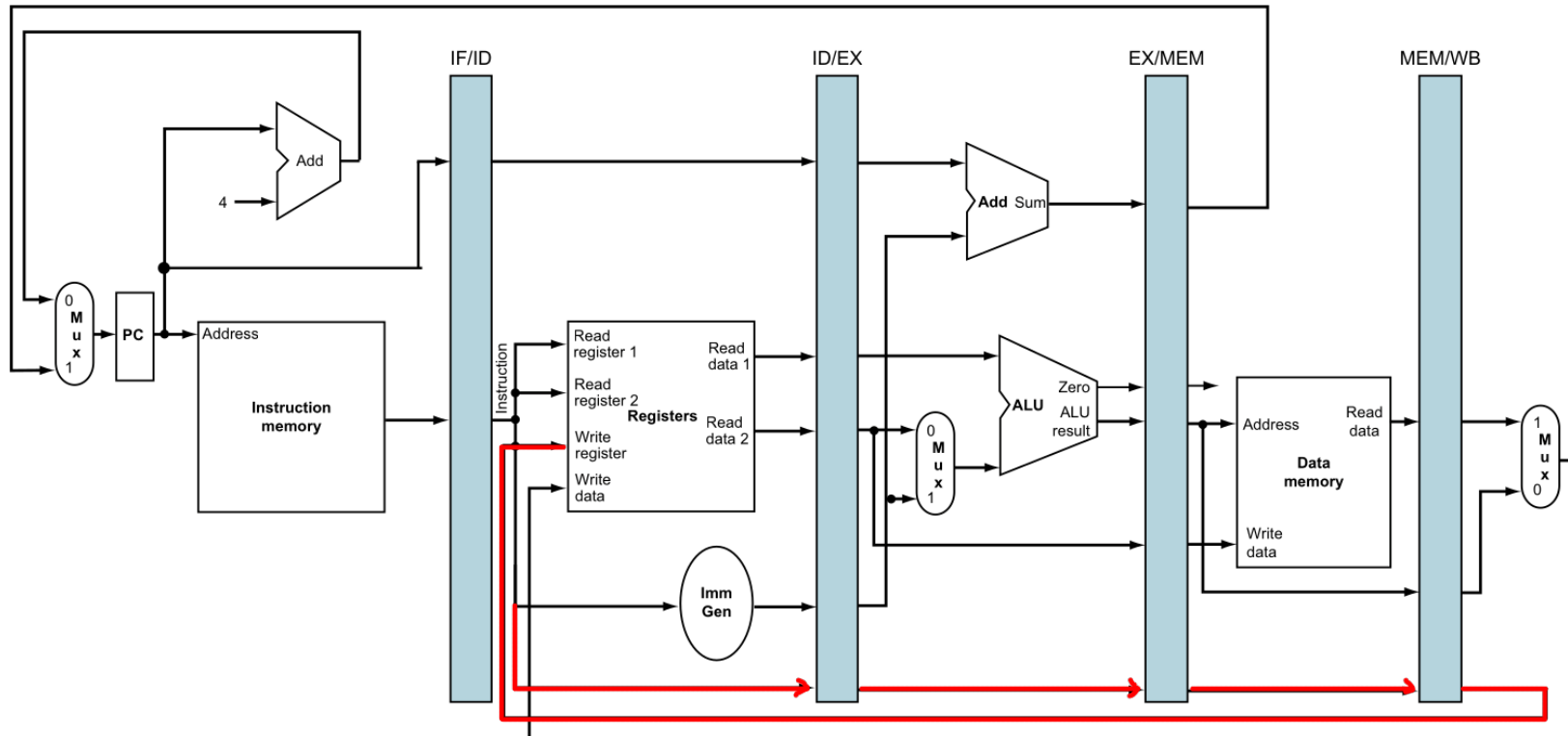 


*datapath for save register id*



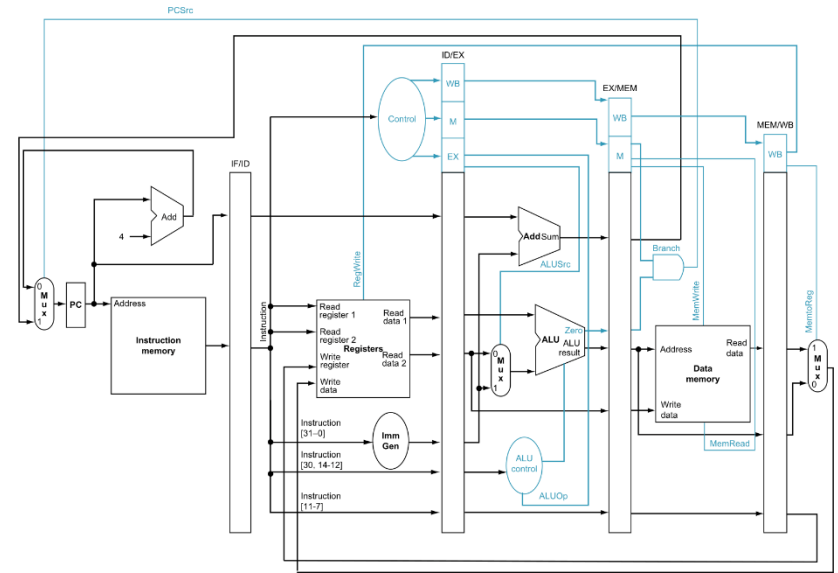

# A Pipelined Control Path


# Pipelined Control (Simplified)

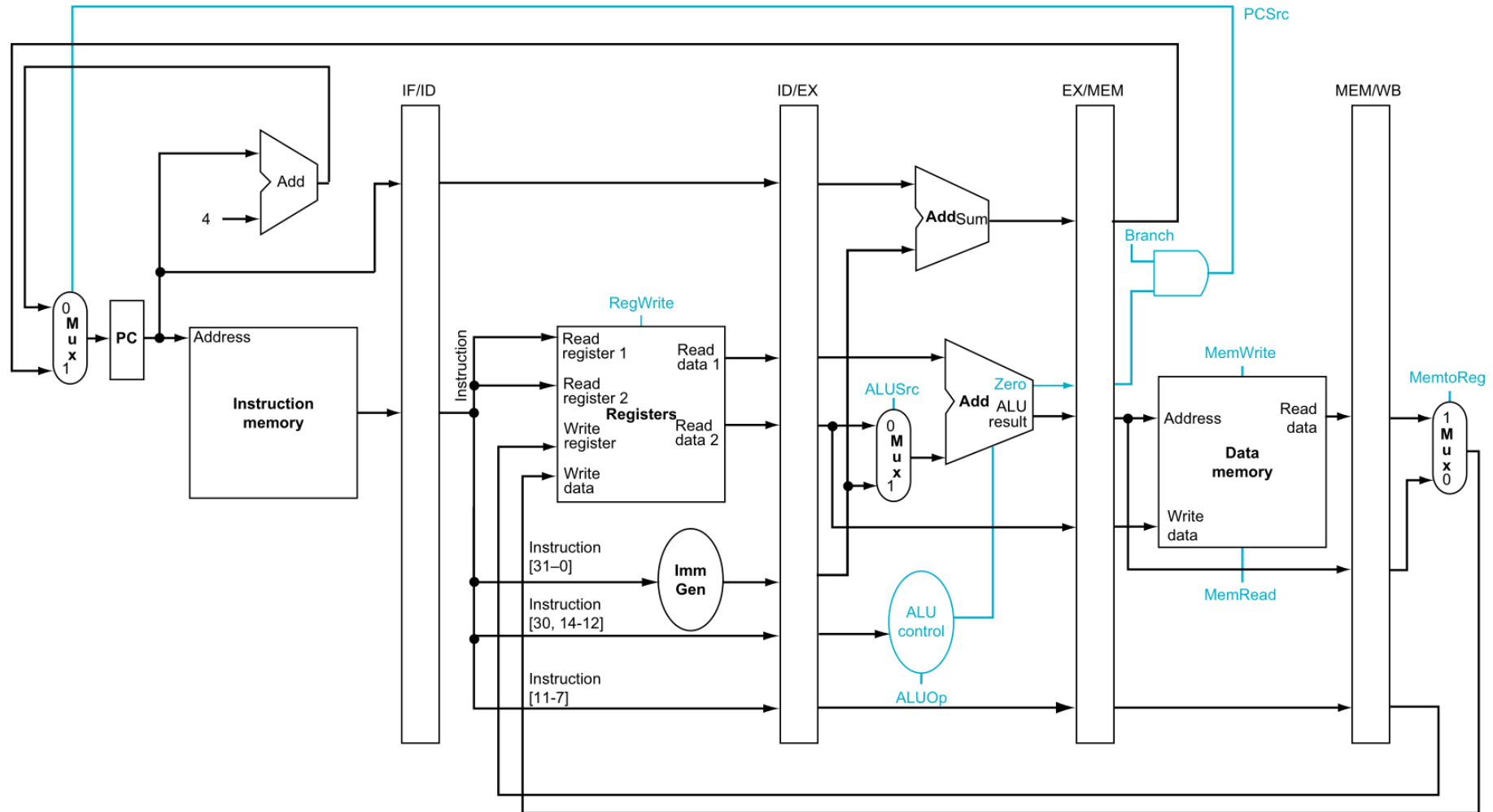

# Control Signals Recap
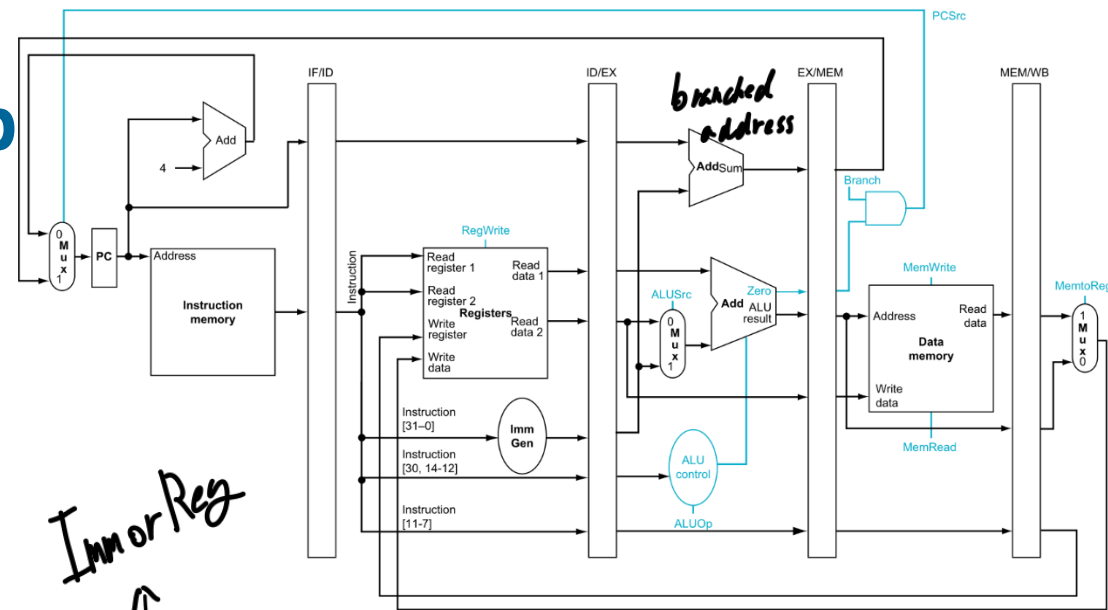
## ■ Six 1-bit control signals

- Same signals as in single-cycle implementation



Signal	Action when Low	Action when High
RegWrite	None	Write value at $Write\ data_{RF}$ port to register[ <i>Write register</i> ]
ALUSrc	Second ALU operand = <i>Read data 2</i>	Second ALU operand = sign-extended, 12 bits of instruction
PCSrc	new PC = old PC + 4	new PC = result of branch target adder
MemRead	None	$Read\ data = mem[Address]$
Mem Write	None	$mem[Address] = Write\ data_{DM}$
MemtoReg	$Write\ data_{RF} = output\ of\ ALU$	$Write\ data_{RF} = output\ of\ data\ memory$

# ALU Control Signals Recap

## ■ Combinational logic derives ALU control

- Input
  - ▶ 2-bit ALUOp derived from opcode field
  - ▶ funct7 and funct3 from instruction
- Output: ALU control

opcode	ALUOp	Operation	funct7	funct3	ALU function	ALU control
lw	00	load register	XXXXXXXX	XXX	add	0010
sw	00	store register	XXXXXXXX	XXX	add	0010
beq	01	branch on equal	XXXXXXXX	XXX	subtract	0110
R-type	10	add	0000000	000	add	0010
		subtract	0100000	000	subtract	0110
		AND	0000000	111	AND	0000
		OR	0000000	110	OR	0001

# Generating Control Signals

*If: None*

*ID: None*

*EX: ALUop/ALUSrc*

*MEM: PCsrc/MemRead/MemWrite*


*WB: MemtoReg/RegWrite*

Instruction	Execution/address calculation stage control lines		Memory access stage control lines			Write-back stage control lines	
	ALUOp	ALUSrc	Branch	Mem-Read	Mem-Write	Reg-Write	Memto-Reg
R-format	10	0	0	0	0	1	0
lw	00	1	0	1	0	1	1
sw	00	1	0	0	1	0	X
beq	01	0	1	0	0	0	X


*Use Imm*
 
# Pipelined Control


- Control signals derived from instruction (ID stage)
  - as in single-cycle implementation
  - conveyed to appropriate stage via pipeline registers



# Pipelined Control

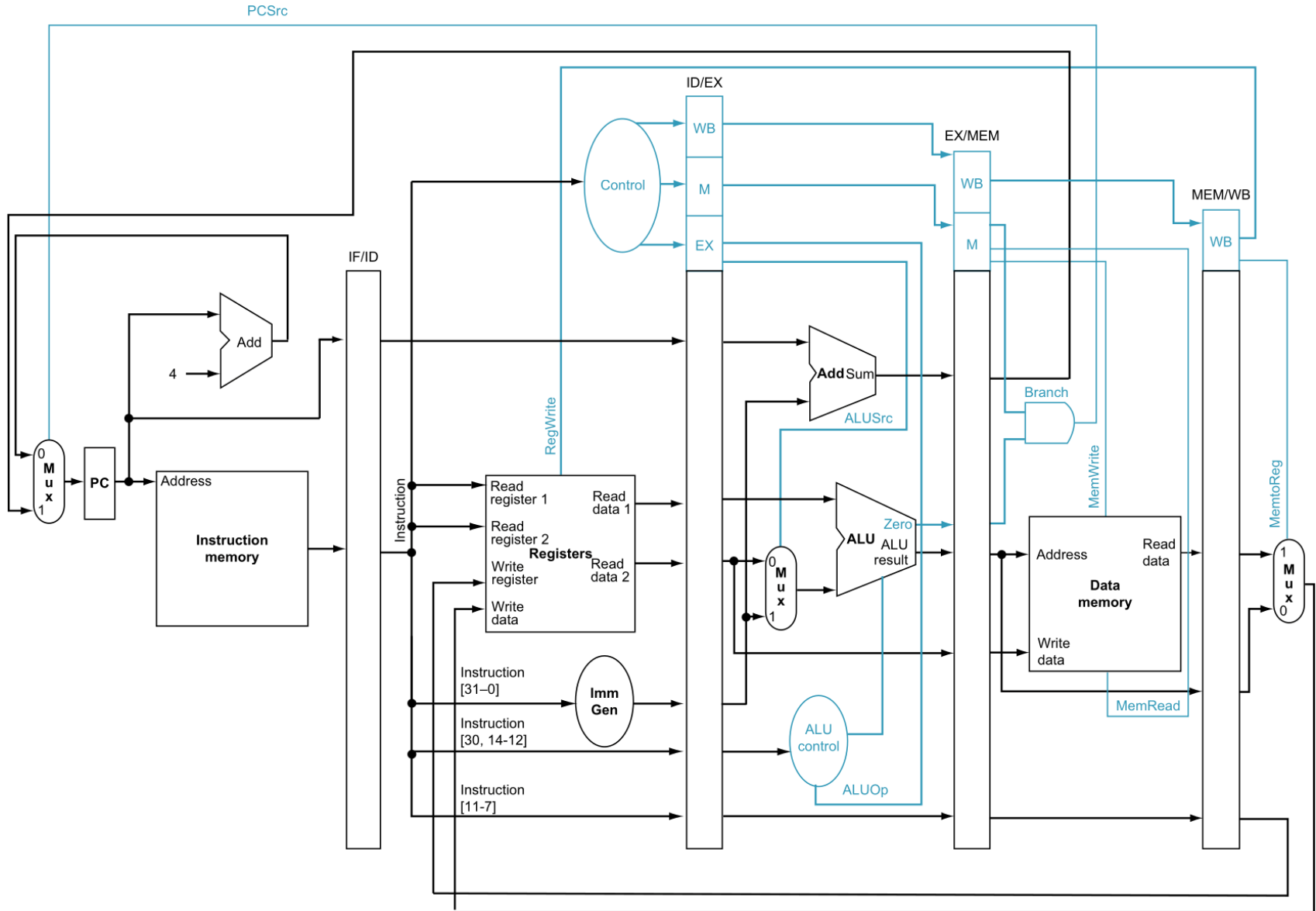

 *RegWrite: write reg or not*  
*MemtoReg: MUXing executed data or memory data*



## Module Summary



# Module Summary

## ■ Pipelined datapath

- Insert pipeline registers between stages
- Forward all data signals one stage per cycle

## ■ Pipelined control path

- Pipelined control identical to single-cycle control
- Control signals forwarded through pipeline registers to respective stage

## ■ Current implementation does not yet handle hazards