 



# Processor Architecture

## 15 min Logic Design Recap



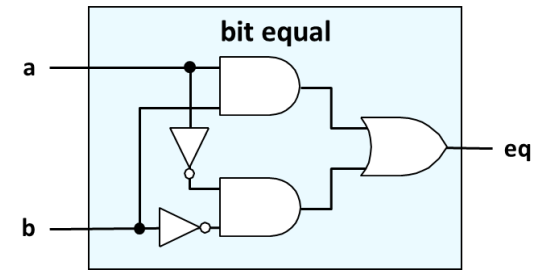
# Module Outline

- **Combinational Circuits**
- **Sequential Circuits**
- **Sequential Operation**
- **Module Summary**




# Combinational Circuits

# Digital Signals

 


- Use **voltage thresholds** to extract discrete values from continuous signal
- Simplest version: 1-bit signal
  - Either high range (1) or low range (0)
  - With guard range between them
- Not strongly affected by noise or low quality circuit elements
  - Can make circuits simple, small, and fast


# Computing with Logic Gates

 

 - Outputs are Boolean functions of inputs
- *Continuously* respond to changes in inputs
  - With some small delay




# Combinational Circuits

 

- Acyclic network of logic gates
    - Continuously responds to changes on inputs
    - Outputs become (after some delay) boolean functions of inputs
-

# Bit Equality Circuit

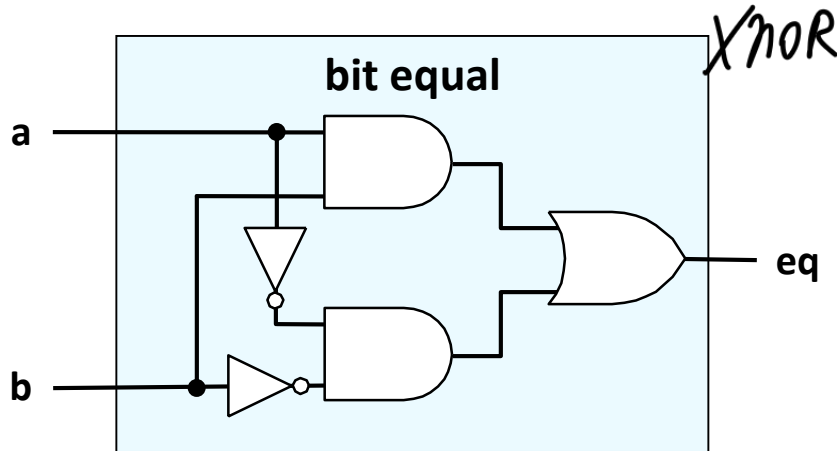

Generate 1 iff a and b are equal


HDL Expression

```
bool eq = (a&&b) || (!a&&!b)
```


## ■ Hardware Description Language (HDL)

- Hardware description language
  - ▶ Boolean operations have syntax similar to C logical operations
- Verilog, VHDL, Bluespec, ...

# Word Equality Circuit

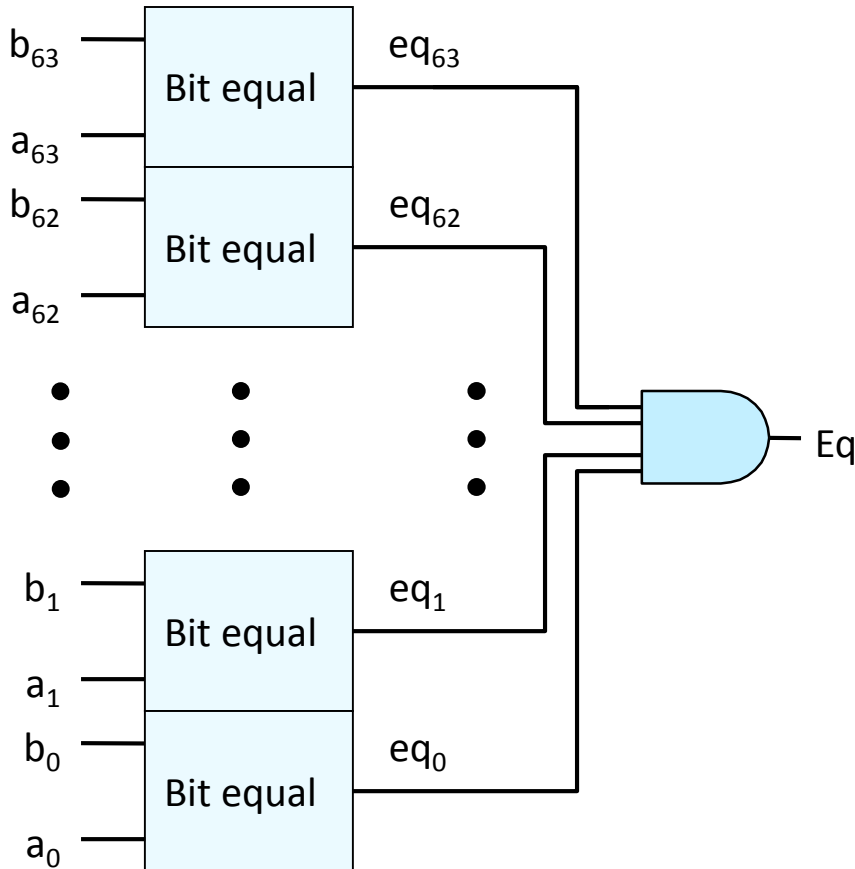

## Word-Level Representation

 


## HDL Representation

```
bool Eq = (A == B)
```

- 64-bit word size
- HDL representation
  - Equality operation
  - Generates Boolean value



# Bit-Level Multiplexor

 

HDL Expression

```
bool out = (s&&a)||(!s&&b)
```


## ■ Input

- Control signal *s*
- Data signals *a* and *b*


## ■ Output

- *s*=1: *a*
- *s*=0: *b*

# Word Multiplexor

 


## Word-Level Representation

 
 
## HDL Representation



```
int Out = [
    s : A;
    1 : B;
];
```

- Select input word A or B depending on control signal  $s$
- HDL representation
  - Case expression
  - Series of test : value pairs
  - Output value of ***first successful test***





# Sequential Circuits

# Registers

  

- Stores word of data *for one cycle*
  - Different from *program registers* seen in assembly code
- Loads input on rising edge of clock
- Acts as barrier between input and output



# Register Operation

  

# State Machine Example


## ■ Accumulator circuit

- Load or accumulate on each cycle

  
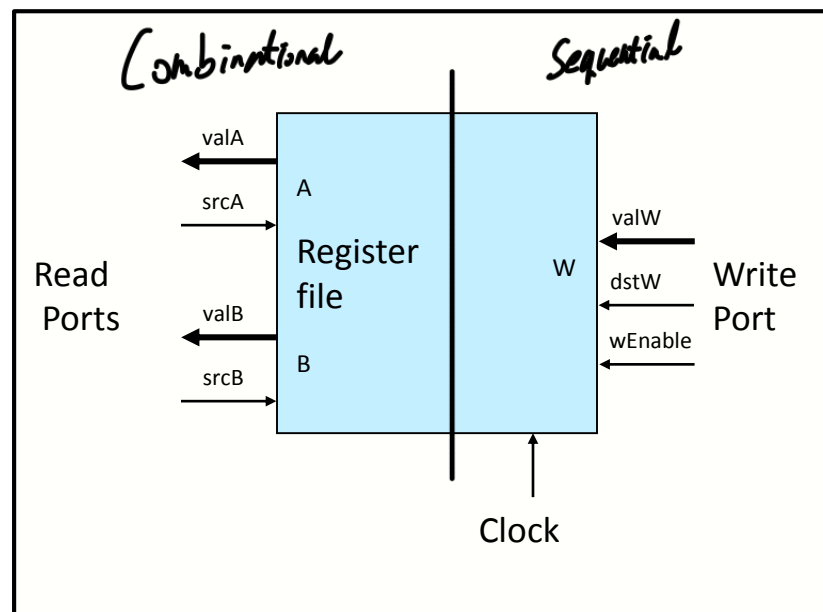
# Random-Access Memory


- Stores multiple words of memory
  - Address input specifies which word to read or write
- Register file
  - Holds values of program registers
  - x1, x2, etc.
  - Register index serves as address
- Multiple Ports
  - Can read and/or write multiple words in one cycle
    - ▶ Each has separate address and data input/output



# Register File Timing

 
## ■ Reading

- Like combinational logic
- Output data generated based on input address (after some delay)



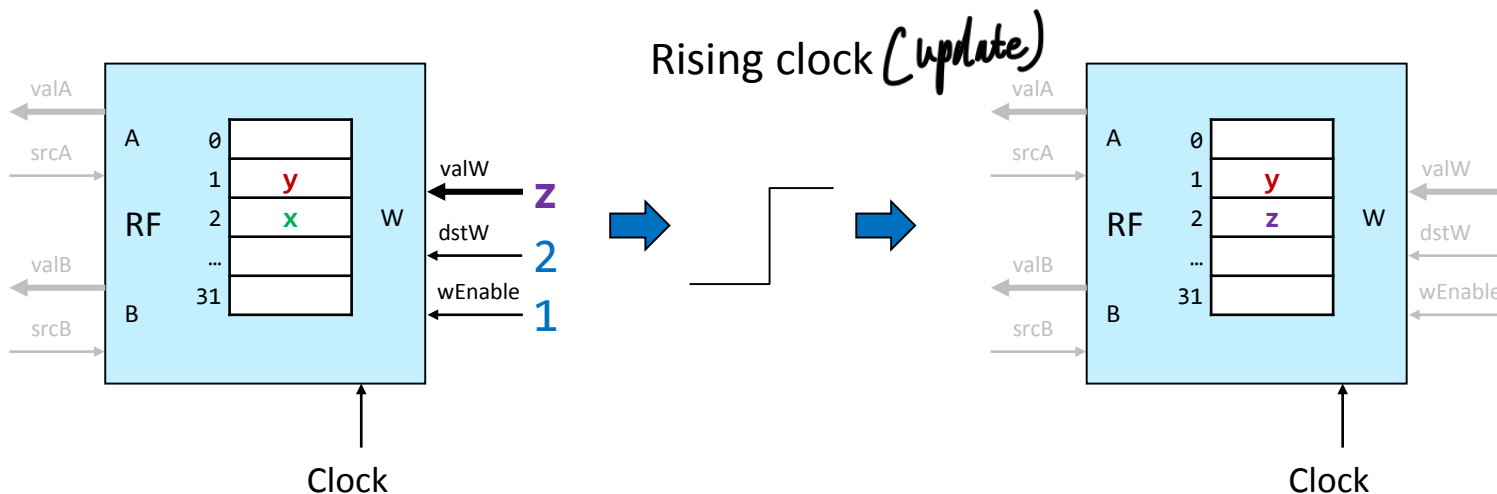
## ■ Writing

- Like register (*Sequential*)
- Update only as clock rises







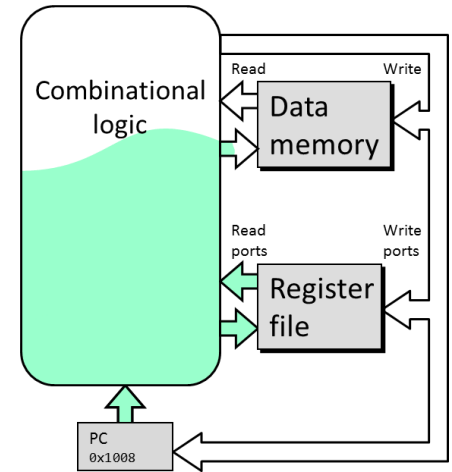



# Sequential Operation
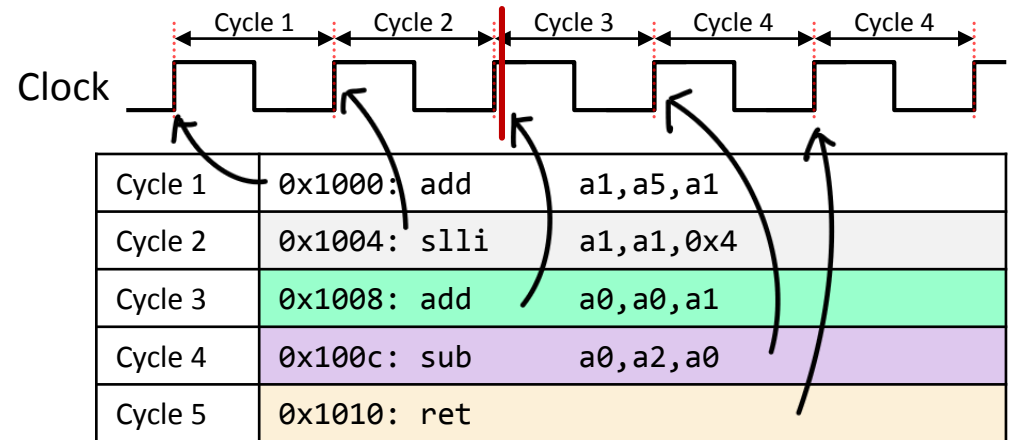 
# Sequential Operation: Executing an Instruction



- Timing: immediately after start of cycle 3 (rising clock edge)
- Combinational logic starting to react to state changes

 
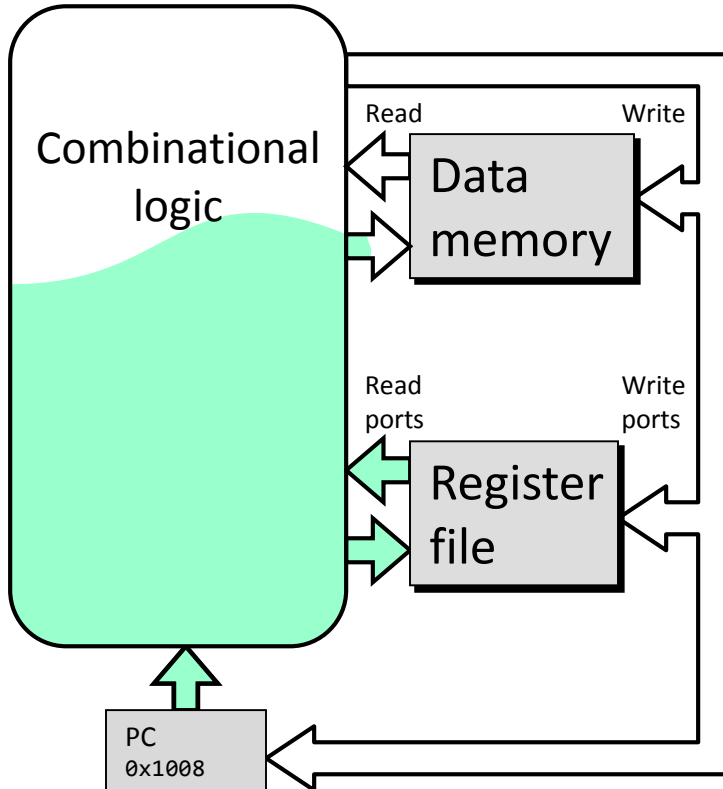
# Sequential Operation: Executing an Instruction



Cycle 1	0x1000: add	a1, a5, a1
Cycle 2	0x1004: slli	a1, a1, 0x4
Cycle 3	0x1008: add	a0, a0, a1
Cycle 4	0x100c: sub	a0, a2, a0
Cycle 5	0x1010: ret	

- Combinational logic generates results for current instruction (add)
- Not all results may have been generated in the middle of the cycle
  
# Sequential Operation: Executing an Instruction





Cycle 1	0x1000: add	a1, a5, a1
Cycle 2	0x1004: slli	a1, a1, 0x4
Cycle 3	0x1008: add	a0, a0, a1
Cycle 4	0x100c: sub	a0, a2, a0
Cycle 5	0x1010: ret	

- Combinational logic generates results for current instruction (add)
- All results must be generated and have arrived at the clocked elements before the end of the cycle


*(waiting for update)*
 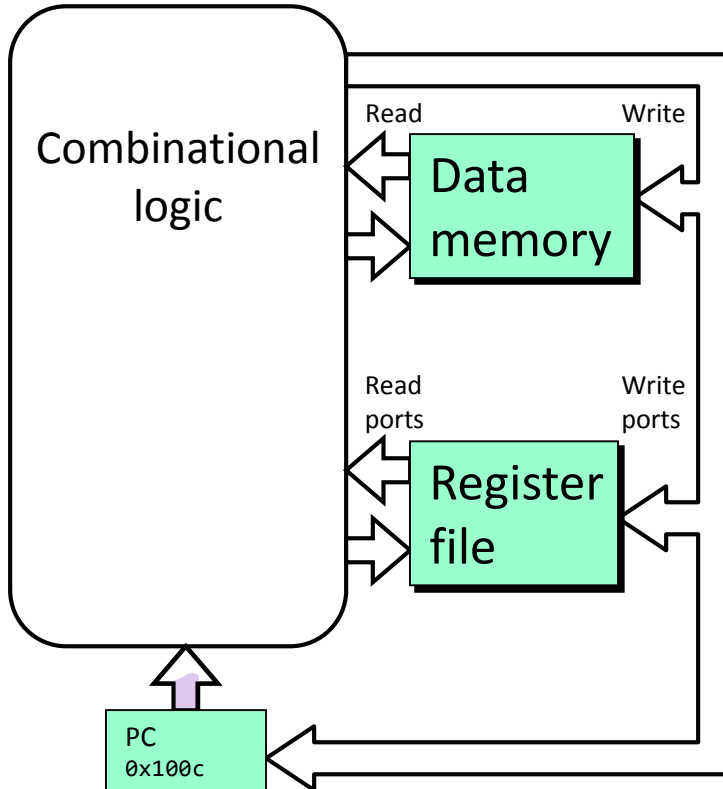
# Sequential Operation: Executing an Instruction



Cycle 1	0x1000: add	a1, a5, a1
Cycle 2	0x1004: slli	a1, a1, 0x4
Cycle 3	0x1008: add	a0, a0, a1
Cycle 4	0x100c: sub	a0, a2, a0
Cycle 5	0x1010: ret	

 - Rising clock edge to start cycle 4
- State set according to add instruction
- Combinational logic starting to react to state changes (=execute next instruction)



# Module Summary

# Module Summary – Logic Design

## ■ Combinational circuits

- Desired operation implemented with a combination of basic logic gates
- Acyclic circuits
- Continuous operation – state propagates from inputs to outputs

## ■ Sequential circuits

- Store state
- State change only in reaction to a particular event
  - ▶ Such as the rising edge of a clock signal

## ■ Processors are made up from a combination of combinational and sequential circuits